

PORTNOTE SOLUTIONS

PWM Dimmer ED **PWM / Power**

Solution Products



CDSOT23-T12C

Design Kit



BOURNS

Europe: *Tel* +41-(0)41 768 55 55

Fax +41-(0)41 768 55 10

Objective

This solution is designed to protect LED dimmer controls with 12 VDC/1 Amp and PWM control signal from overcurrent, overvoltage, ESD and surge events.

Solution

1 Multifuse[®] PPTC Resettable Fuse: MF-MSMF110/16-2 2 TVS Diode Arrays: CDSOT23-T12C

Compliance


IEC61000-4-2 ESD Level 4 (8 kV / 15 kV) IEC61000-4-4 EFT IEC61000-4-5 Surge / Lightning

Alternate Recommendations

Solutions are available for lower/higher levels of overvoltage/overcurrent protection

Benefit

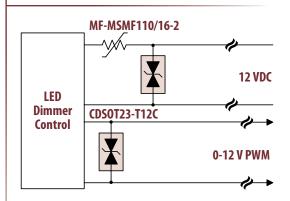This solution provides ESD/EFT/surge and supplies overcurrent protection from potential faults during installation within rated limits.



The schematic above illustrates the application protection and does not constitute the complete circuit design. Customers should verify actual device performance in their specific applications.

Americas: *Tel* +1-951 781-5500 *Fax* +1-951 781-5700

Asia-Pacific: *Tel* +886-2 256 241 17 Fax +886-2 256 241 16 Bourns[®] PortNote[®] solutions provide protection recommendations for typical port threats.

> For more information, go to: www.bourns.com or email: protection@bourns.com

COPYRIGHT© 2012 • BOURNS, INC. • 6/12 • e/CPK1144 • "PortNote" is a registered service mark of Bourns, Inc. "Bourns" and "Multifuse" are registered trademarks of Bourns, Inc. in the U.S. and other countries.