

SLIC Protection

ITU-T 4kV Solution, Dual Supply Voltage

Bourns[®] PortNote[®] solutions provide protection recommendations for typical port threats.

Solution Products



TISP9110MDMR-S



CMF-RL55-10-0

Objective

The SLIC (Subscriber Line Interface Circuit) provides all the BORSCHT functions such as battery, ringing and supervision between the codec and telephone handset.

This PortNote[®] solution provides protection recommendations for SLIC interfaces against 4 kV 10/700 μ s surge and power contact threats.

Solution

1 Thyristor: TISP9110MDMR-S

2 CPTC Resettable Fuses: CMF-RL55-10-0

Compliance

ITU-T Basic for K.20, K.21, K.45

- Increased surge withstand level to 10/700 μ s, 4 kV without primary protection


Alternate Recommendations

Other PortNote[®] Solutions:

- SLIC Protection: GR-1089-Core Solution, Dual Supply Voltage
- SLIC Protection: ITU-T Basic Solution, Dual Supply Voltage

Benefit

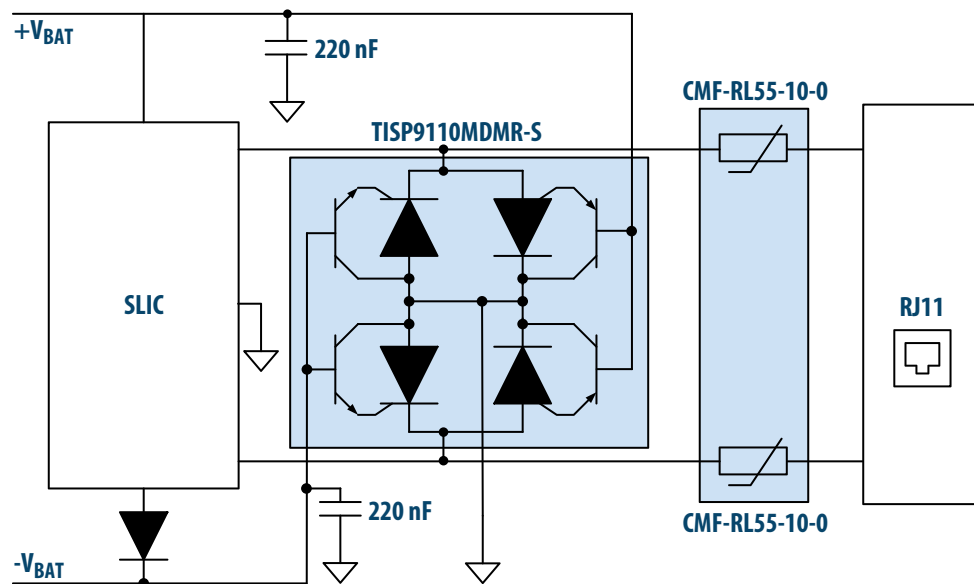This solution provide a 4 kV 10/700 μ s level of protection in dual voltage ringing SLIC with a smaller PCB space.



The schematic above illustrates the application protection and does not constitute the complete circuit design. Customers should verify actual device performance in their specific applications.

Request Sample 

To order samples, click on the "Request Sample" button.

www.bourns.com

BOURNS[®]

Americas: Tel +1-951 781-5500
Email americus@bourns.com

EMEA: Tel +36 88 520 390
Email eurocus@bourns.com

Asia-Pacific: Tel +886-2 256 241 17
Email asiacus@bourns.com